

Practical #1

- 1) Use Cadence Virtuoso to draw the transistor-level schematic of an inverter (NOT gate).
- 2) Use Cadence Virtuoso to draw the transistor-level schematic of a NAND gate.