

Practical #2

- a) Please use Synopsys HSPICE to simulate the behavior and performance of your inverter, which you have drawn for Practical #1 by using Cadence Virtuoso.